

Lecture 7

Monday, 31 August 2009
10:36 AM

Open ckt Test

-measure V_1, V_2, I, P

$$\therefore \frac{N_1}{N_2} = \frac{V_1}{V_2}$$

$$R_0 = \frac{V_1^2}{P}$$

$$S = VI$$



$$Q = \sqrt{S^2 - P^2}$$

$$X_0 = \frac{V_1^2}{Q}$$

Short ckt test

with the terminals of winding 2 s/cct increase the applied voltage on winding 1 until rated primary current flows at rated frequency.

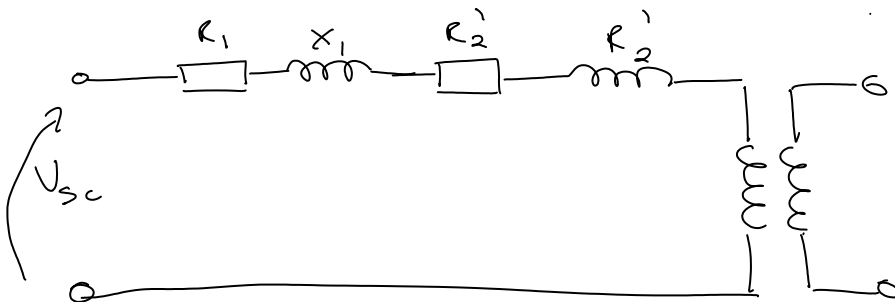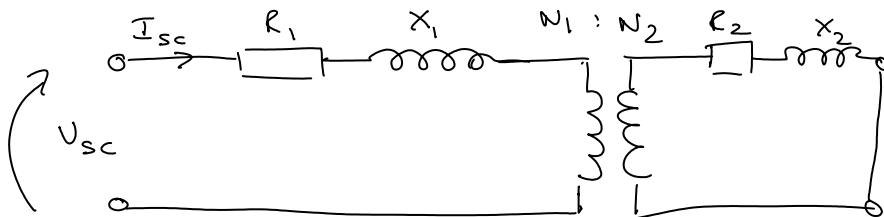Since R_0, X_0 are very much higher than the winding impedance the exciting current may be ignored



$$R_T = R_1 + R_2' = R_1 + a R_2$$

$$X_T = X_1 + X_2' = X_1 + a X_2$$

take measurements of V_{sc}, I_{sc}, P_{sc}

take measurements of V_{sc} , I_{sc} , P_{sc}

$$P_{sc} = I_{sc}^2 R_T \quad \therefore R_T = \frac{P_{sc}}{I_{sc}^2}$$

$$S_{sc} = V_{sc} I_{sc}$$

$$Q_{sc} = \sqrt{S_{sc}^2 - P_{sc}^2}$$

$$\therefore X_T = \frac{Q_{sc}}{I_{sc}^2}$$


it is usually assumed that $X_1 = X_2' = \frac{1}{2} X_T$

\Rightarrow leakage flux paths are the same for each winding

$$X_1 = \omega L_1 = \frac{\omega N_1^2}{R_l}$$

$$X_2 = \omega L_2 = \frac{\omega N_2^2}{R_l}$$
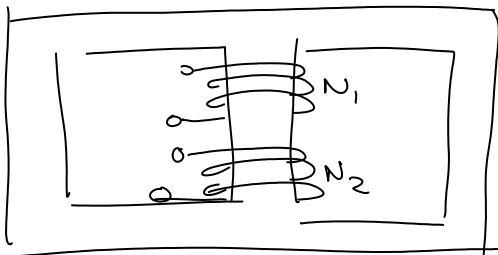
$$\begin{aligned} X_2' &= \left(\frac{N_1}{N_2}\right)^2 X_2 \\ &= \left(\frac{N_1}{N_2}\right)^2 \frac{\omega N_2^2}{R_l} \\ &= \frac{\omega N_1^2}{R_l} = X_1 \end{aligned}$$



$$L_1 = \frac{N_1^2}{R_L} \quad L_2 = \frac{N_2^2}{R_L}$$

$$L_2' = \left(\frac{N_1}{N_2} \right)^2 \times \left(\frac{N_2^2}{R_L} \right)$$

$$= \frac{N_1^2}{R_L}$$

Winding resistance measurements.

R_1 & R_2 may be measured directly using d.c.


This will give the DC resistance only and may be different to AC resistance (due to skin effect).

$$R_{oc} = R_{1oc} + \left(\frac{N_1}{N_2} \right)^2 R_{2oc}$$

if the values of R_T & R_{DC} vary appreciably, then the AC winding resistance could be divided into the ratio of the DC resistance 3 windings.

Transformer Phase Diagrams

Approximate Equivalent CCT. V_w

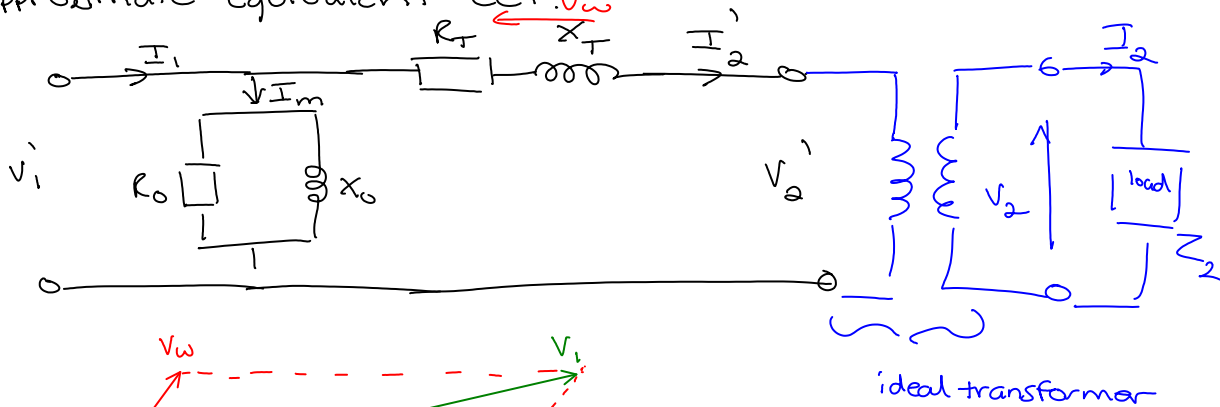

Transformer Efficiency

$$\text{Efficiency } (\eta) = \frac{\text{output power}}{\text{input power}}$$

$$\begin{aligned} \text{Efficiency } (\eta) &= \frac{\text{output power}}{\text{input power}} \\ &= \frac{\text{output power}}{\text{output power} + \text{losses}} \\ &= \frac{\text{input power} - \text{losses}}{\text{input power}}. \end{aligned}$$

can get v high efficiency

efficiency is a function of the load and the power factor so these quantities must be stated when the efficiency is stated.

eg $\eta = 0$ for zero load.

$\eta \rightarrow 1$ for loads near to the transformer rating.

usually quoted as a %

can't measure the difference between input and output power for v high η so can't use $\frac{\text{output power}}{\text{input power}}$.

hence we need to determine the losses independently.

Losses in R_0 & R_T
 \uparrow core loss \uparrow winding loss

core losses are constant ie independant of load.

$$P_c = \frac{V_1^2}{R_0} \quad \text{fixed loss}$$

winding losses are dependant on load.

$$P_w = I_2^2 R_T \quad \text{variable loss}$$

Core Losses

$$P_c = \frac{V_1^2}{R_0} \quad \text{watts.}$$

should be constant for a given V_1

may be determined through open ckt test

Winding losses

$$P_w = (I_2')^2 R_T \text{ (watts)}$$

this is a function of the operating condition and may be determined for any given operating condition.

let the secondary load be

$$P_{out} = V_2' I_2' \cos \phi_2$$

$$\Rightarrow \eta = \frac{V_2' I_2' \cos \phi_2}{V_2' I_2' \cos \phi_2 + P_c + (I_2')^2 R_T}$$

